



**BERKELEY LAB**  
Bringing Science Solutions to the World



U.S. DEPARTMENT OF  
**ENERGY**

# How a Buck Converter Works

Evan Mladina


Student Instrumentation Meeting -- March 20, 2020


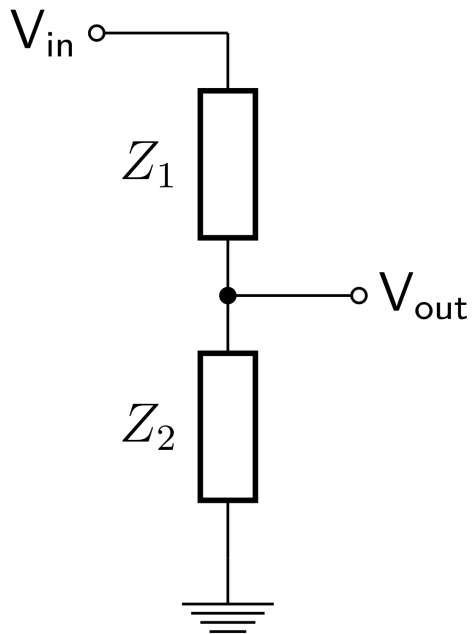
# DCDC Converters

- **Linear Regulators**


Uses a series of resistors to drop down voltage by dissipating heat.



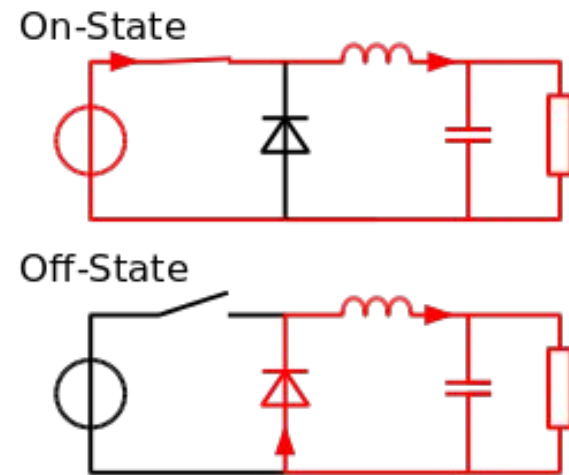Example: Voltage divider

- **Switching Regulators**


Uses a series of switches to step down (or up) the average output voltage.




Example: Buck converter
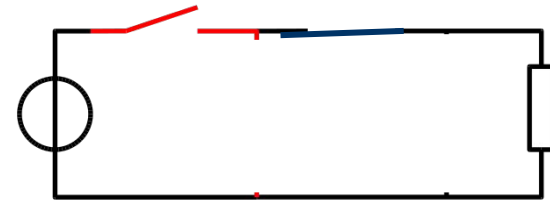
# Building up a Buck Converter

Start with a simple circuit with a switch. When looking at voltages we are looking at the average voltage. In this case we get a ripple the size of the input voltage.




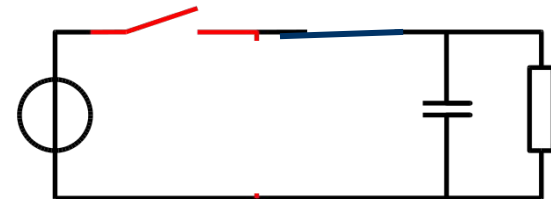Add capacitor to flatten out the voltage, making it closer to the average. However, switching the current on instantaneously can fry the circuit.



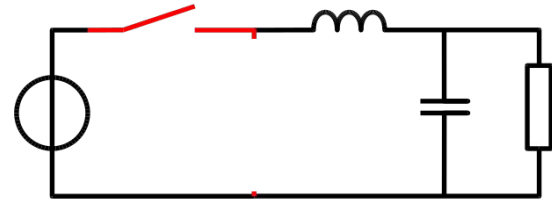
# Building up a Buck Converter cont.

We can add inductor to help slow down the instantaneous flow of current. However, when the switch opens, a large negative voltage develops, which could potentially cause a spark.



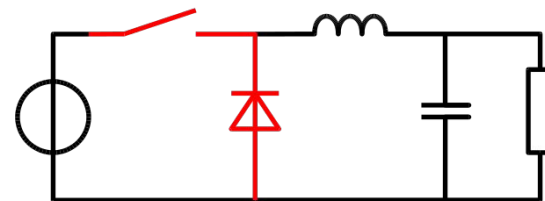
We can add a diode allowing a place for the charge to go.





# Current flow through a buck converter

- With the switch closed, the diode is reverse biased, allowing current to flow through the inductor.
- The current increases until the switch is opened.
- The inductor keeps pushing current through, but the voltage across it switches, forward biasing the diode.

On-State

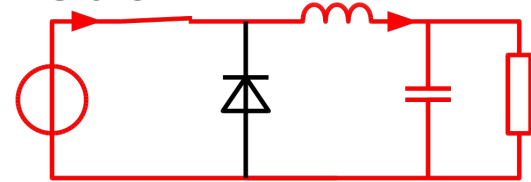


Off-State

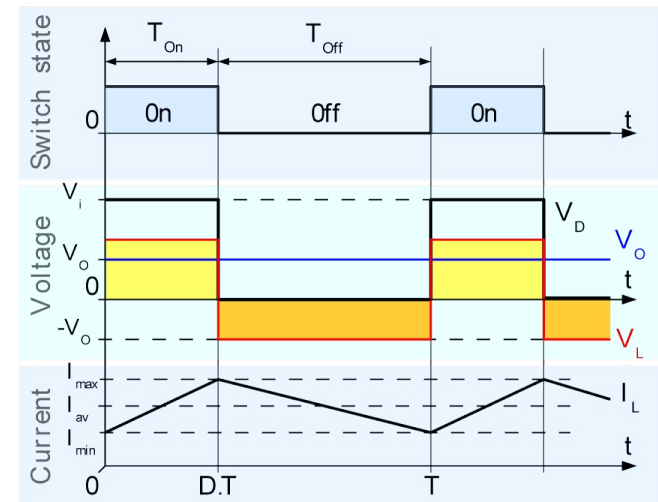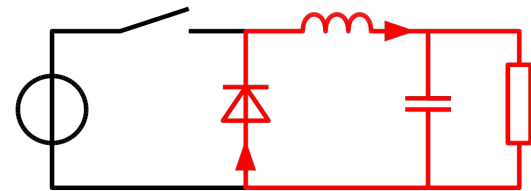
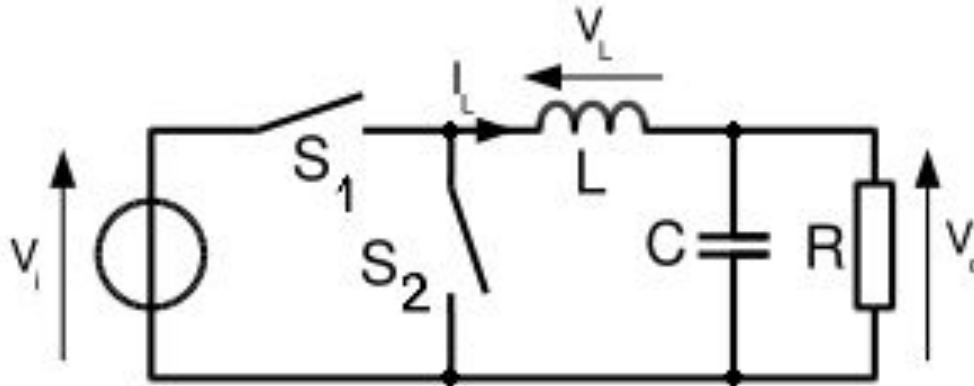
# Powerboard FEAST

The FEAST replaces the diode with another switch. The two switches open and close opposite each other. This is often done as the power loss across the second switch is less than across a diode.



# Output voltage transfer function


- For the case with just a switch, power supply, and load clearly the average output is equal to the duty cycle times the input voltage.
- For the full buck converter it can be shown that the output voltage is given by the same equation.

$$D = \frac{V_o}{V_i}$$


$$t_{\text{on}} = DT$$
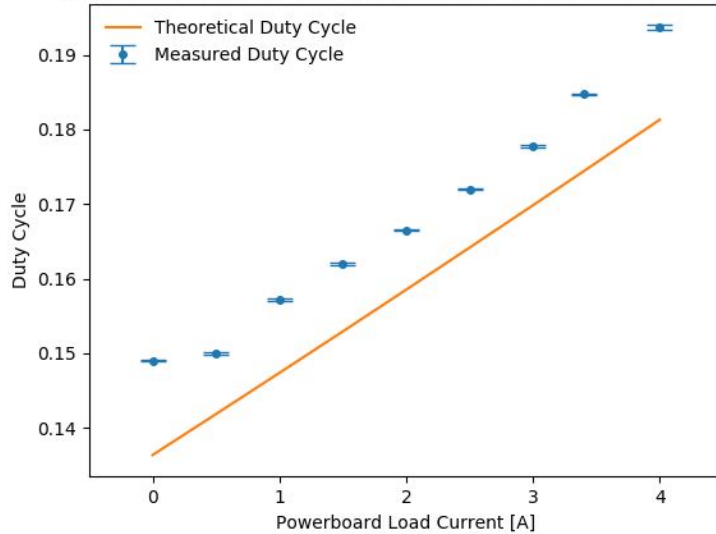
# Non Ideal duty cycle

FEAST Duty Cycle at -20C with 11V input voltage on Powerboard



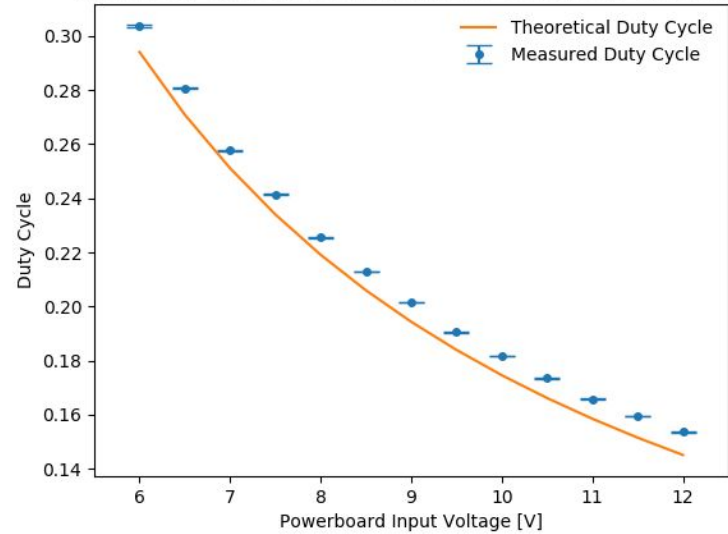FEAST Duty Cycle at -20C with 2A Load Current on Powerboard




$$D = \frac{V_o + (V_{sw, sync} + V_L)}{V_i - V_{sw} + V_{sw, sync}}$$

- $V_{sw}$  is the voltage drop on the power switch,
- $V_{sw, sync}$  is the voltage drop on the synchronous switch or diode
- $V_L$  is the voltage drop on the inductor.


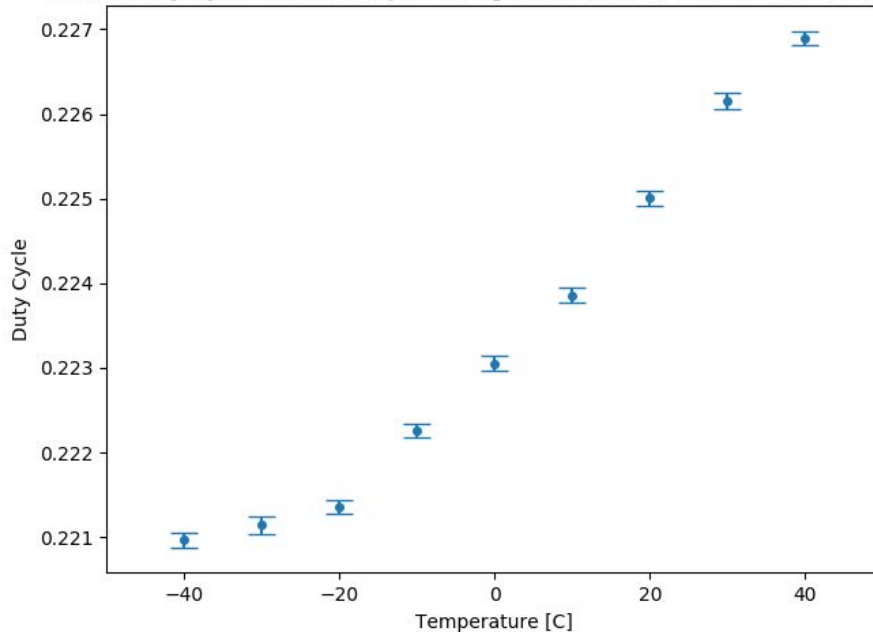
# Temperature effects on the duty cycle

FEAST Duty Cycle with 11V Input Voltage and 2A Load Current on Powerboard



$$D = \frac{V_o + (V_{sw, sync} + V_L)}{V_i - V_{sw} + V_{sw, sync}}$$

- As the temperature increases, so does the resistance of the two switches and the coil.
- With a set output voltage, input voltage, and load current, we see from the above equation that the duty cycle can only increase.